

Name: _____

CWID: _____

Calculators Not Allowed
No Work = No Credit
Write Legibly

Question	Points	Score
1	10	
2	10	
Total:	20	

1. 10 points An experimentalist observes a particle of charge q , mass m , and energy qV_o moving in a circular orbit of radius r_o inside a **spherical** capacitor with inner radius a and outer radius b , see Fig. (1).

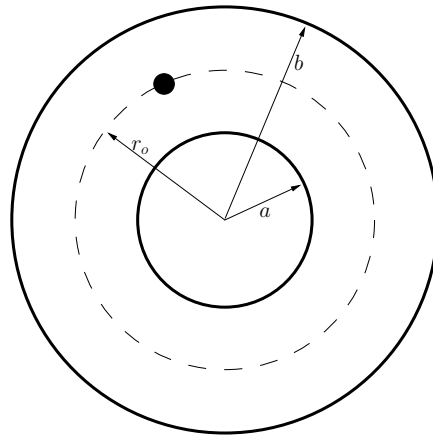


Figure 1: A particle of charge q , mass m , and energy qV_o moving inside a **spherical** capacitor is shown.

The experimentalist quickly observes that the particle only moves in a circular orbit with radius r_o when $V_a - V_b$ has a very special value. Find this value. **Start with Gauss's Law.**

Solution: Let Q be the amount of positive charge on the inner sphere; the electric field between the two spheres is given by (use Gauss's Law to show this or look at the Recitation 2 problems)

$$E = \frac{Q}{4\pi\epsilon_o r^2}, \quad a < r < b, \quad (1)$$

The electric potential difference, $V_a - V_b$, is given by (see Recitation 2 problems)

$$\begin{aligned}
 V_a - V_b &= \int_a^b \vec{E} \cdot d\vec{\ell} \\
 &= \int_a^b \vec{E} \cdot dx\hat{i} \\
 &= \int_a^b E dx \\
 &= \frac{Q}{4\pi\epsilon_o} \int_a^b \frac{1}{x^2} dx \\
 &= \frac{Q}{4\pi\epsilon_o} \left(\frac{b-a}{ab} \right).
 \end{aligned}$$

Thus,

$$Q = \frac{4\pi\epsilon_o ab}{(b-a)} (V_a - V_b). \quad (2)$$

Setting the particle's kinetic energy equal to qV_o yields

$$v^2 = \frac{2qV_o}{m}, \quad (3)$$

where v is the particle's speed. Finally, using (1), (2), (3), and Newton's Second Law yields

$$\begin{aligned}
 qE &= m \frac{v^2}{r_o} \\
 q \left[\frac{4\pi\epsilon_o ab}{(b-a)} (V_a - V_b) \right] \left[\frac{1}{4\pi\epsilon_o r_o^2} \right] &= \frac{m}{r_o} \left[\frac{2qV_o}{m} \right] \\
 V_a - V_b &= \frac{2V_o r_o (b-a)}{ab}
 \end{aligned}$$

Table 1: **For Grader Use Only:** Rough grading criteria are given below.

Computation of E field	3 pts
Computation of $V_a - V_b$	3 pts
Energy of the particle, $\frac{mv^2}{2} = qV_o$	2 pts
Newton's Law and algebra	2 pts

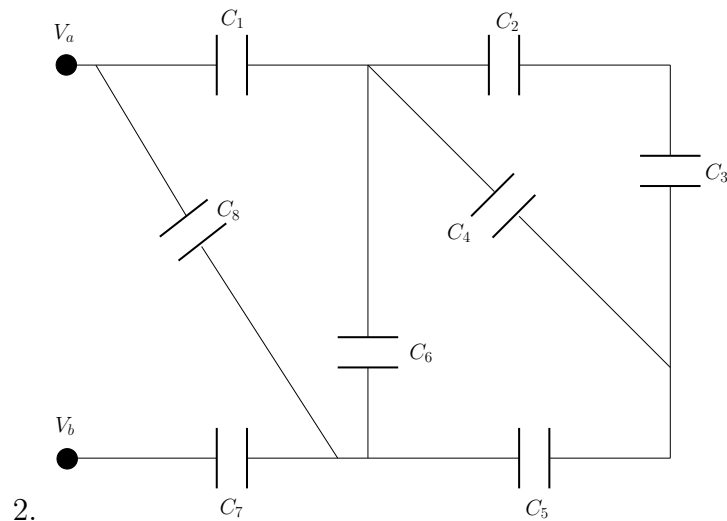


Figure 2: A capacitor network is shown.

- (a) 7 points Find the equivalent capacitance, C_{eq} , of the circuit shown in Fig. (2). You may use \perp , \parallel symbolism.

Solution:

$$C_9 = C_2 \perp C_3 \quad (4)$$

$$C_{10} = C_9 \parallel C_4 \quad (5)$$

$$C_{11} = C_5 \perp C_{10} \quad (6)$$

$$C_{12} = C_6 \parallel C_{11} \quad (7)$$

$$C_{13} = C_1 \perp C_{12} \quad (8)$$

$$C_{14} = C_8 \parallel C_{13} \quad (9)$$

$$C_{\text{eq}} = C_{14} \perp C_7 \quad (10)$$

Table 2: **For Grader Use Only:** Rough grading criteria are given below.

Each numbered equation	1 pt
------------------------	------

- (b) 3 points Give formulas for computing $a \perp b$ and $a \parallel b$.

Solution:

$$a \perp b = (a^{-1} + b^{-1})^{-1} \quad (11)$$

$$a \parallel b = a + b \quad (12)$$

Table 3: **For Grader Use Only:** Rough grading criteria are given below.

Each numbered equation	1.5 pts
------------------------	---------